 


# Assignment 6

## 1. Preparation tasks

Timing diagram figure for displaying value '3.142'



## 2. Display driver

Listing of VHDL code of the process p\_mux

```
p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i, dp_i)
begin
    case s_cnt is
        when "11" =>
            s_hex <= data3_i;
            dp_o <= dp_i(3);
            dig_o <= "0111";
        when "10" =>
            s_hex <= data2_i;
            dp_o <= dp_i(2);
            dig_o <= "1011";
        when "01" =>
            s_hex <= data1_i;
            dp_o <= dp_i(1);
            dig_o <= "1101";
        when others =>
            s_hex <= data0_i;
            dp_o <= dp_i(0);
            dig_o <= "1110";
        end case;
    end process p_mux;
```

Listing of VHDL testbench file tb\_driver\_7seg\_4digits

```
--
-- Template for 4-digit 7-segment display driver testbench.
-- Nexys A7-50T, Vivado v2020.1.1, EDA Playground
--
-- Copyright (c) 2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----
library ieee;
use ieee.std_logic_1164.all;
-----
-- Entity declaration for testbench
-----
entity tb_driver_7seg_4digits is
    -- Entity of testbench is always empty
end entity tb_driver_7seg_4digits;
-----
-- Architecture body for testbench
-----
architecture testbench of tb_driver_7seg_4digits is
    -- Local constants
    constant c_CLK_100MHZ_PERIOD : time := 10 ns;
    --Local signals
    signal s_clk_100MHz : std_logic;
    signal s_reset : std_logic;
    signal s_data0 : std_logic_vector(4 - 1 downto 0);
    signal s_data1 : std_logic_vector(4 - 1 downto 0);
    signal s_data2 : std_logic_vector(4 - 1 downto 0);
    signal s_data3 : std_logic_vector(4 - 1 downto 0);
    signal s_dp_i : std_logic_vector(4 - 1 downto 0);
    signal s_dp_o : std_logic;
    signal s_seg : std_logic_vector(7 - 1 downto 0);
    signal s_dig : std_logic_vector(4 - 1 downto 0);

begin
    -- Connecting testbench signals with driver_7seg_4digits entity
    -- (Unit Under Test)
    uut_driver_7seg_4digits : entity work.driver_7seg_4digits
    port map (
        clk => s_clk_100MHz,
        reset => s_reset,
        data0_i => s_data0,
        data1_i => s_data1,
        data2_i => s_data2,
        data3_i => s_data3,
        dp_i => s_dp_i,
        dp_o => s_dp_o,
        seg_o => s_seg,
        dig_o => s_dig
    );

    -- Clock generation process

    p_clk_gen : process
    begin
        while now < 750 ns loop -- 75 periods of 100MHz clock
            s_clk_100MHz <= '0';
            wait for c_CLK_100MHZ_PERIOD / 2;
            s_clk_100MHz <= '1';
            wait for c_CLK_100MHZ_PERIOD / 2;
        end loop;
        wait;
    end process p_clk_gen;

    -- Reset generation process

    p_reset_gen : process
    begin
        s_reset <= '0';
        wait for 10 ns;
        -- Reset activated
        s_reset <= '1';
        wait for 53 ns;
        -- Reset deactivated
        s_reset <= '0';
        wait;
    end process p_reset_gen;

    -- Data generation process

    p_stimulus : process
    begin
        report "Stimulus process started" severity note;

        -- 3.142

        s_data3 <= "0011";
        s_data2 <= "0001";
        s_data1 <= "0100";
        s_data0 <= "0010";
        s_dp_i <= "0111";

        report "Stimulus process finished" severity note;
        wait;
    end process p_stimulus;

end architecture testbench;
```

Screenshots with simulated time waveforms



Listing of VHDL architecture of the top layer

```
entity top is
    Port ( CLK100MHz : in std_logic; --Main Clock
          BTNC : in std_logic; --Synchronous reset
          CA : out std_logic; --Cathod A
          CB : out std_logic; --Cathod B
          CC : out std_logic; --Cathod C
          CD : out std_logic; --Cathod D
          CE : out std_logic; --Cathod E
          CF : out std_logic; --Cathod F
          CG : out std_logic; --Cathod G
          DP : out std_logic; --Decimal point
          AN : out std_logic_vector(8 - 1 downto 0)); --Common anode signals to individual displays
end top;

architecture Behavioral of top is
begin
    -- Instance (copy) of driver_7seg_4digits entity
    driver_seg_4 : entity work.driver_7seg_4digits
    port map
    (
        clk => CLK100MHz,
        reset => BTNC,
        data0_i(3) => SW(3),
        data0_i(2) => SW(2),
        data0_i(1) => SW(1),
        data0_i(0) => SW(0),

        data1_i(3) => SW(7),
        data1_i(2) => SW(6),
        data1_i(1) => SW(5),
        data1_i(0) => SW(4),

        data2_i(3) => SW(11),
        data2_i(2) => SW(10),
        data2_i(1) => SW(9),
        data2_i(0) => SW(8),

        data3_i(3) => SW(15),
        data3_i(2) => SW(14),
        data3_i(1) => SW(13),
        data3_i(0) => SW(12),

        seg_o(6) => CA,
        seg_o(5) => CB,
        seg_o(4) => CC,
        seg_o(3) => CD,
        seg_o(2) => CE,
        seg_o(1) => CF,
        seg_o(0) => CG,

        dig_o => AN(4 - 1 downto 0),
        dp_i => "0111",
        dp_o => DP
    );
end architecture Behavioral;
```

## 3. Eight-digit driver

Image of the driver schematic

