

Assignment 5

1. Preparation tasks

Figure with connection of push buttons on Nexys A7 board

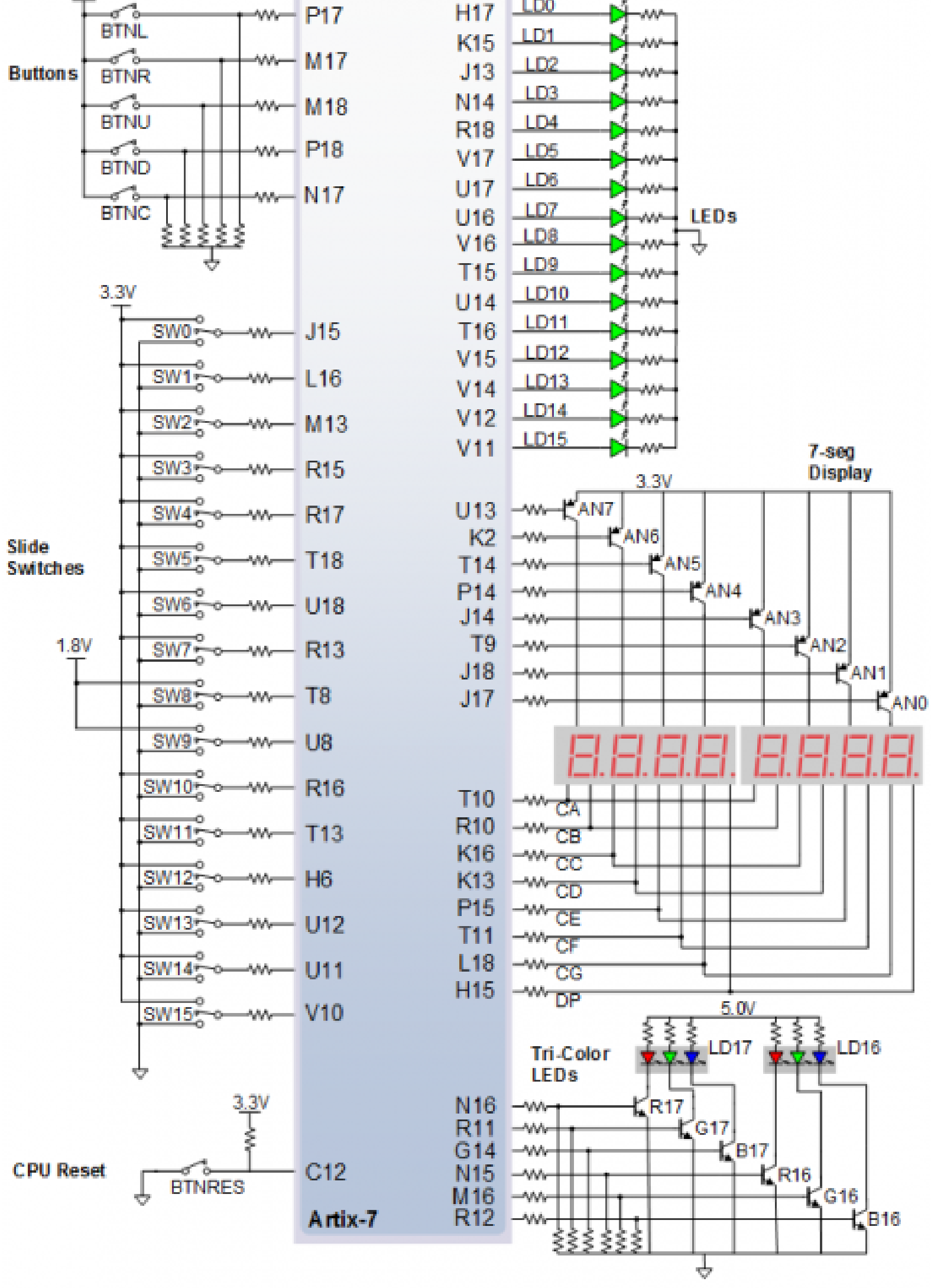


Table with calculated values

Time interval	Number of clk periods	Number of clk periods in hex	Number of clk periods in binary
2 ms	200 000	x"3_0D40"	b"0011_0000_1101_0100_0000"
4 ms	400 000	x"6_1A80"	b"0110_0001_1010_1000_0000"
10 ms	1 000 000	x"F_4240"	b"1111_0100_0010_0100_0000"
250 ms	25 000 000	x"17D_7840"	b"0001_0111_1101_0111_1000_0100_0000"
500 ms	50 000 000	x"2FA_F080"	b"0010_1111_1010_1111_0000_1000_0000"
1 sec	100 000 000	x"5F5_E100"	b"0101_1111_0101_1110_0001_0000_0000"

2. Bidirectional counter

Listing of VHDL code of the process p_cnt_up_down

```
p_cnt_up_down : process(clk)
begin
    if rising_edge(clk) then

        if (reset = '1') then          -- Synchronous reset
            s_cnt_local <= (others => '0'); -- Clear all bits

        elsif (en_i = '1') then        -- Test if counter is enabled

            -- TEST COUNTER DIRECTION HERE
            if (cnt_up_i = '1') then
                s_cnt_local <= s_cnt_local + 1;
            elsif (cnt_up_i = '0') then
                s_cnt_local <= s_cnt_local - 1;
            end if;
        end if;
    end if;
end process p_cnt_up_down;
```

Listing of VHDL reset and stimulus processes from testbench file tb_cnt_up_down.vhd

```
p_reset_gen : process
begin
    s_reset <= '0';
    wait for 12 ns;

    -- Reset activated
    s_reset <= '1';
    wait for 73 ns;

    s_reset <= '0';
    wait;
end process p_reset_gen;

-- Data generation process
-----

p_stimulus : process
begin
    report "Stimulus process started" severity note;

    -- Enable counting
    s_en <= '1';

    -- Change counter direction
    s_cnt_up <= '1';
    wait for 380 ns;
    s_cnt_up <= '0';
    wait for 320 ns;


    -- Disable counting
    s_en <= '0';

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;


end architecture testbench;
```

Screenshots with simulated time waveforms


Full scale

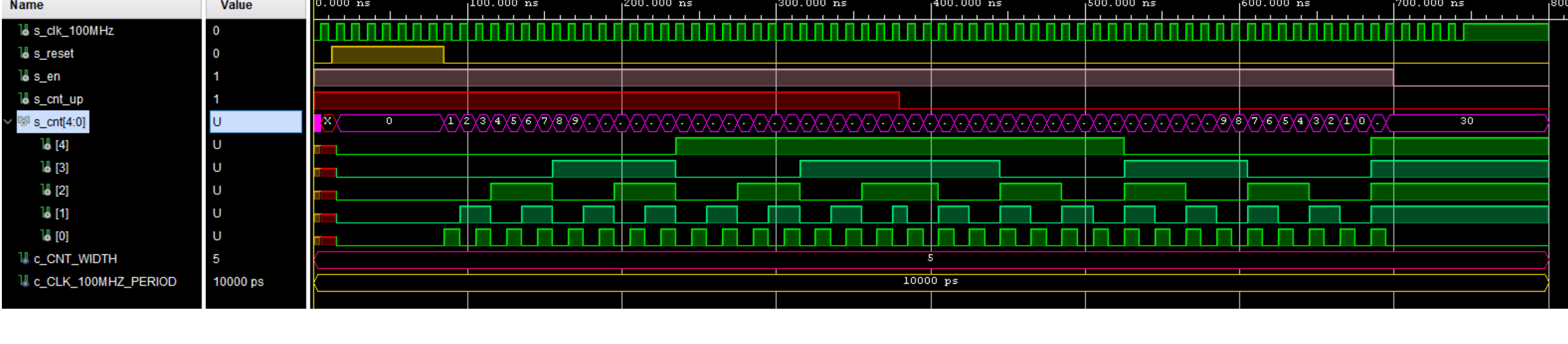


0-260ns

 


260-500ns

 

500-760ns

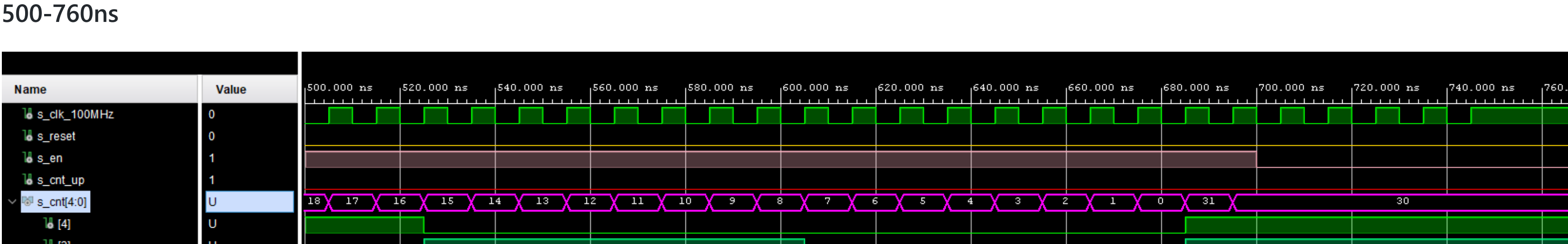

-800ns

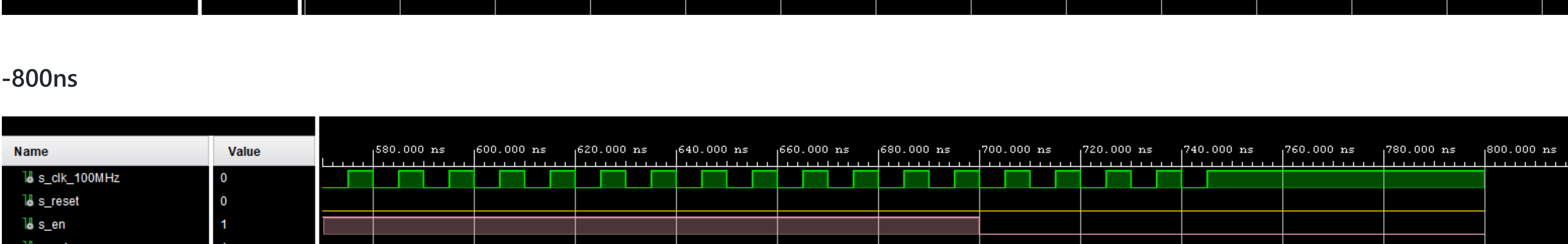

3. Top level

Listing of VHDL code from source file top.vhd

```
-- Instance (copy) of clock_enable entity
clk_en0 : entity work.clock_enable
generic map(
    g_MAX => 100000000
)
port map(
    clk => CLK100MHZ,
    reset => BTNC,
    ce_o => s_en
);

-- Instance (copy) of cnt_up_down entity
bin_cnt0 : entity work.cnt_up_down
generic map(
    g_CNT_WIDTH => 4
)
port map(
    clk => CLK100MHZ,
    reset => BTNC,
    en_i => s_en,
    cnt_up_i => SW(0),
    cnt_o => s_cnt
);

-- Display input value on LEDs
LED(3 downto 0) <= s_cnt;

-- Instance (copy) of hex_7seg entity
hex2seg : entity work.hex_7seg
port map(
    hex_i => s_cnt,
    seg_o(6) => CA,
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
    seg_o(0) => CG
);
```

Image of the top layer including both counters

